

Lecture 3

Digital circuits, power supplies and regulation




Graphics used with permission from AspenCore (<http://electronics-tutorials.ws>)

Agenda

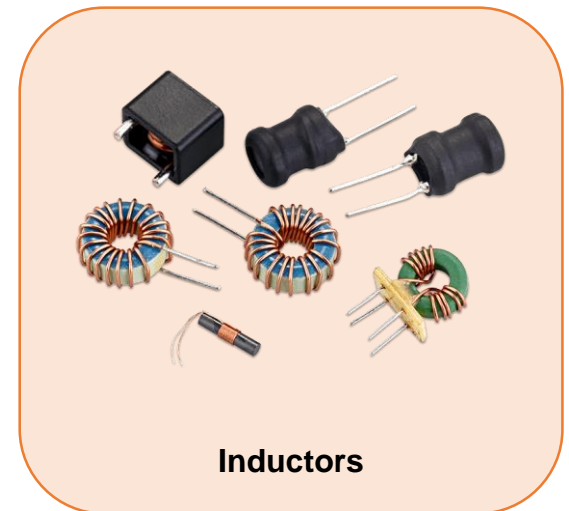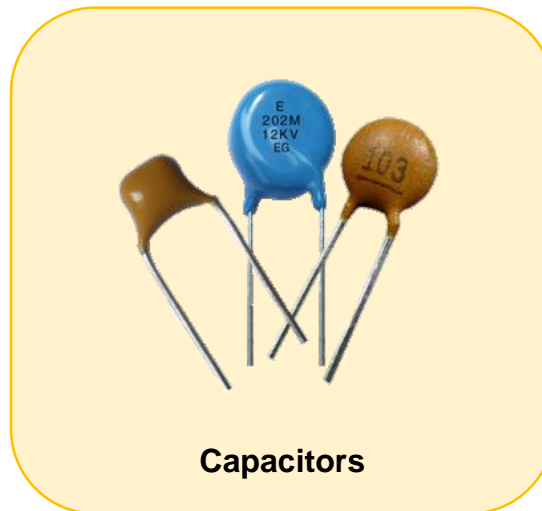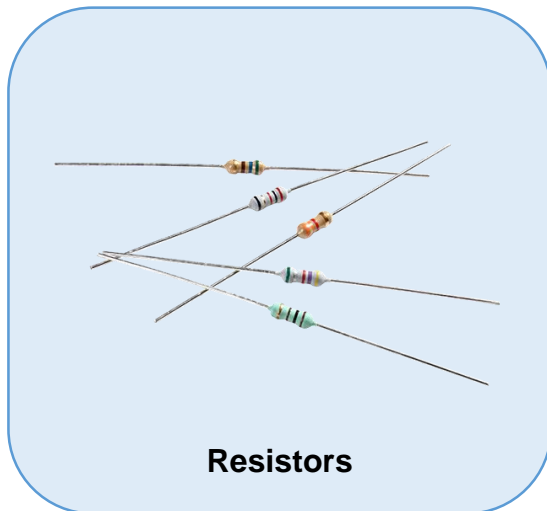1. Review
2. The digital abstraction: logic gates and flip-flops
3. Power supplies and regulation
4. Design project overview
5. Lab 3 overview

Review: Lecture 1 and Lab 1

- Voltage and current: think **pressure** and **flow**
- Ohm's Law: resistor current is linear, **$V = IR$**
- Capacitors and inductors: **energy storage** elements
- Capacitors block **low frequencies**, inductors block **high frequencies**





Review: Lecture 2 and Lab 2

- **Filter:** Response depends on the frequency of the input
- **Diode:** One-way device, current from anode to cathode
- **BJT:** Current-controlled amplifier
- **MOSFET:** Voltage-controlled switch
- **Op-amp:** Performs mathematical operations



Types of filters

LPF

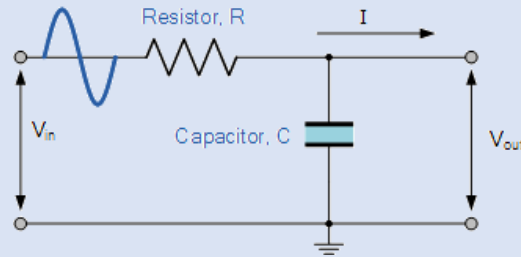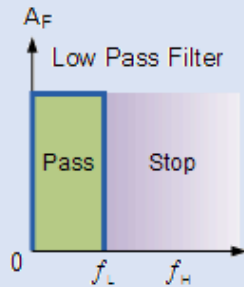



$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

HPF

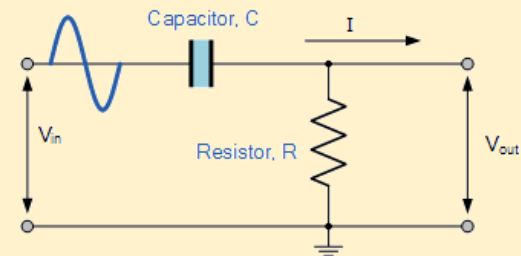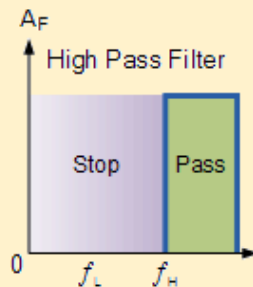

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

BPF

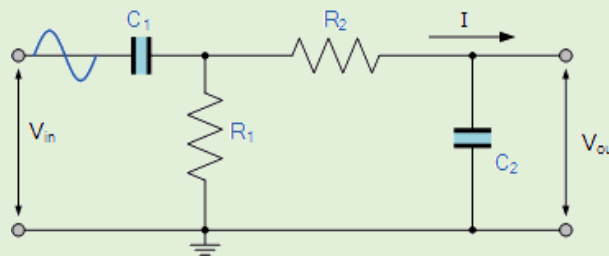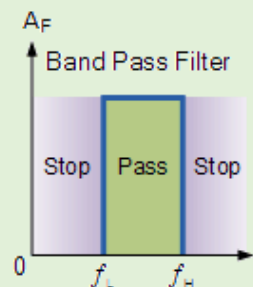

$$f_H = \frac{1}{2\pi R_1 C_1} \text{ Hz}$$

$$f_L = \frac{1}{2\pi R_2 C_2} \text{ Hz}$$


The digital abstraction

Logic gates and flip-flops

Analog vs. digital


Analog

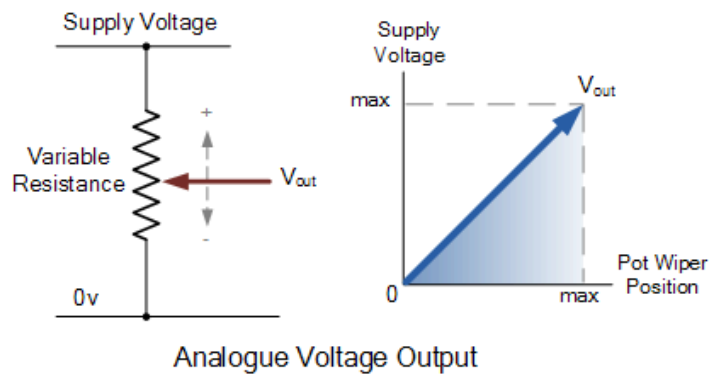- Continuous
- Sensitive to noise
- Modular design difficult



Digital

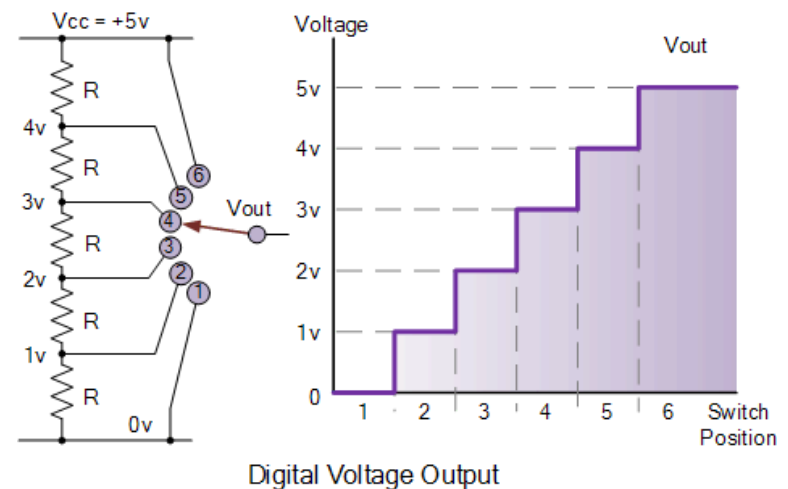- Discrete
- Noise-resistant
- Modular design easy





Binary numbers

- **Binary:** represents numbers as 1's and 0's
- Enables us to perform computations with digital circuits
- Conversion to decimal: n th bit worth 2^n

Bit	7	6	5	4	3	2	1	0	
Value	128	64	32	16	8	4	2	1	
Example 1	1	1	1	1	1	1	1	1	=
	128 +	64 +	32 +	16 +	8 +	4 +	2 +	1	<div>255 (sum)</div>
Example 2	0	1	1	1	0	1	0	1	=
	0 +	64 +	32 +	16 +	0 +	4 +	0 +	1	<div>117 (sum)</div>

Combinational logic

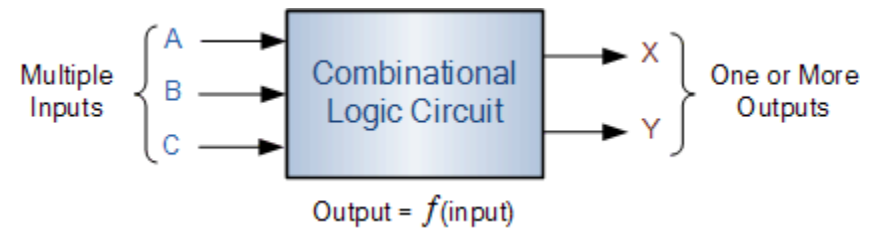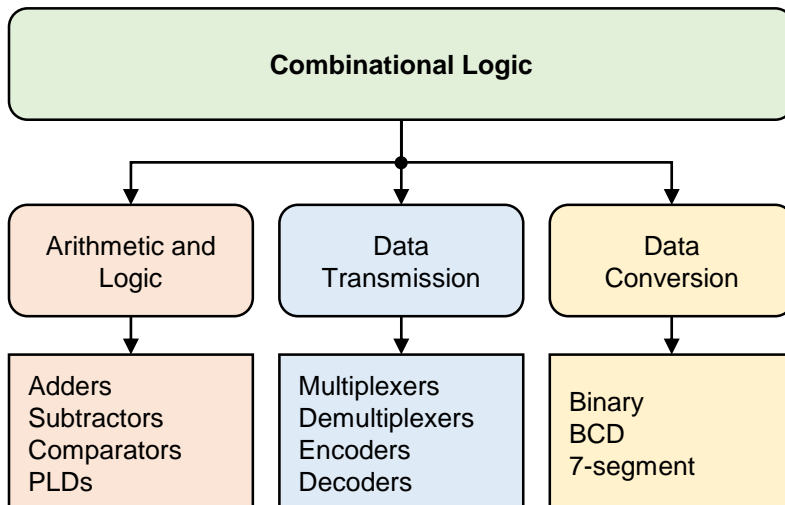
- **Combinational logic circuit:** Output is a function of its inputs, independent of time
- Constructed from basic elements called **gates**




AND gate

- **AND gate:** Output is 1 (“high”) when all inputs are 1
- Equivalent to “**multiplication**”: denoted by asterisk (*) or period (.)

2-input AND gate truth table

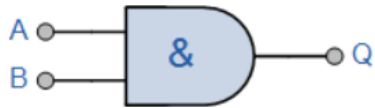Symbol	Truth Table		
 2-input AND Gate	B	A	Q
	0	0	0
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = A.B$	Read as A AND B gives Q		


74LS08 Quad 2-input AND gate

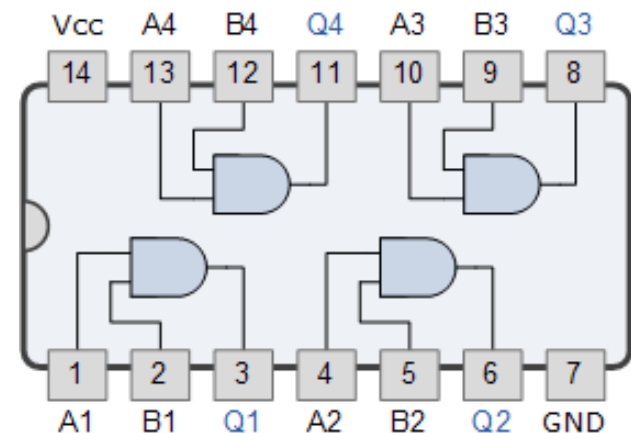


OR gate

- **OR gate:** Output is 1 when at least 1 input is 1
- Equivalent to “**addition**”: denoted by plus sign (+)

2-input OR gate truth table

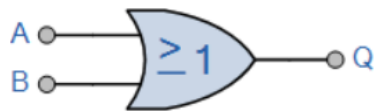Symbol	Truth Table		
 2-input OR Gate	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	1
Boolean Expression $Q = A+B$		Read as A OR B gives Q	


74LS32 Quad 2-input OR gate

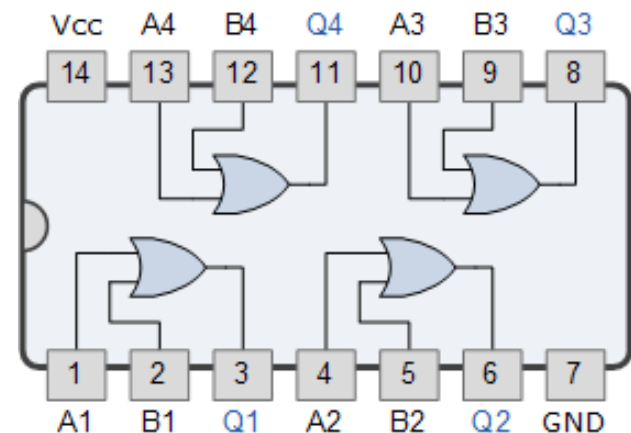


NOT gate

- **NOT gate:** single input, output is “inverse” of input
- Denoted by a horizontal line (not $A = \bar{A}$)
- Inverted outputs and inputs denoted by small “**bubble**”

NOT gate truth table

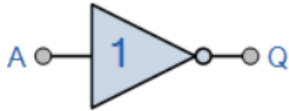Symbol	Truth Table	
 Inverter or NOT Gate	A	Q
	0	1
	1	0
Boolean Expression $Q = \text{not } A$ or \bar{A}	Read as inverse of A gives Q	


74LS04 Hex NOT gate (inverter)

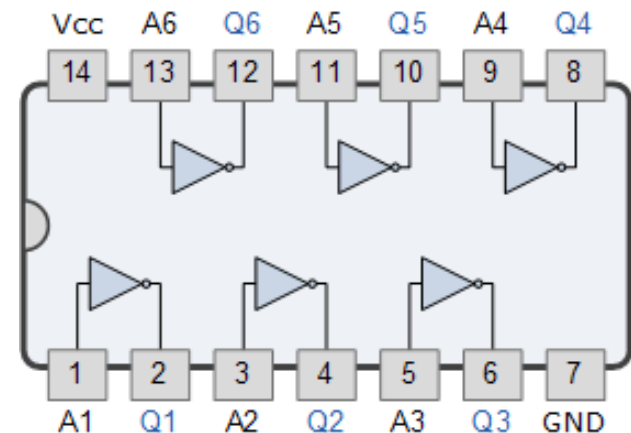


NAND gate

- **NAND gate:** Output is 0 when all inputs are 1
- Same as an AND gate followed by an inverter
- NAND gate is “universal”: any function can be constructed using only NAND gates

2-input NAND gate truth table

Symbol	Truth Table		
 2-input NAND Gate	B	A	Q
	0	0	1
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = \overline{A \cdot B}$		Read as A AND B gives NOT Q	


74LS00 Quad 2-input NAND gate

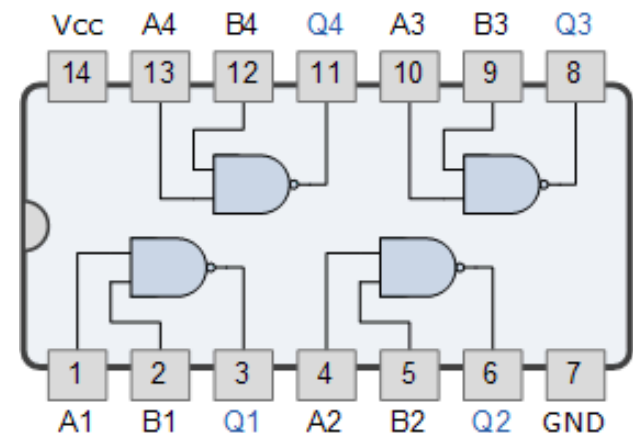


NOR gate

- **NOR gate:** Output is 0 when at least 1 input is 1
- Same as an OR gate followed by an inverter
- NOR gate is “universal”: any function can be constructed using only NOR gates

2-input NOR gate truth table

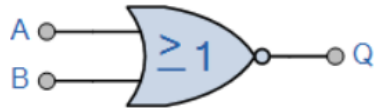Symbol	Truth Table		
 2-input NOR Gate	B	A	Q
	0	0	1
	0	1	0
	1	0	0
	1	1	0
Boolean Expression $Q = \overline{A+B}$		Read as A OR B gives NOT Q	


74LS02 Quad 2-input NOR gate

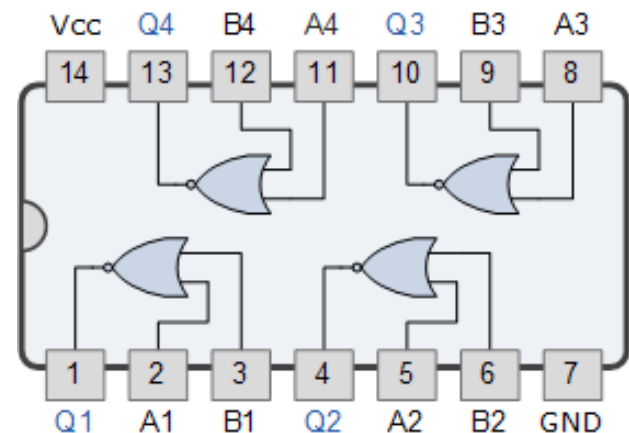


XOR gate

- **XOR gate:** Output is 1 when one (but not 2) input is 1
- XOR = “exclusive OR”: output is only 1 when inputs are different from each other

2-input XOR gate truth table

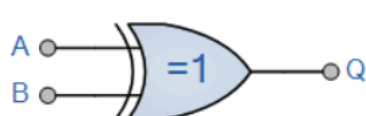
Symbol	Truth Table		
 2-input Ex-OR Gate	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = A \oplus B$	A OR B but NOT BOTH gives Q		

74LS86 Quad 2-input XOR gate

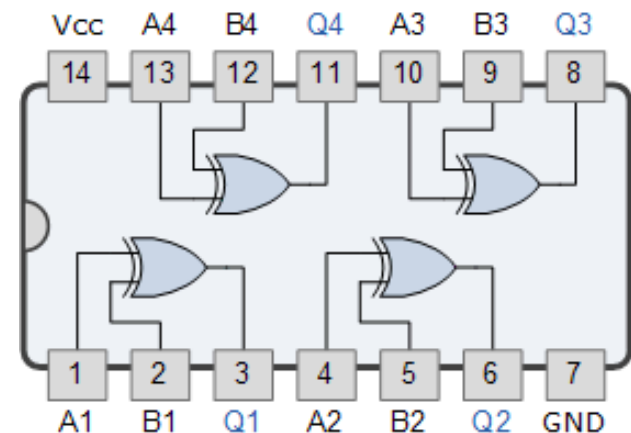

Sequential logic

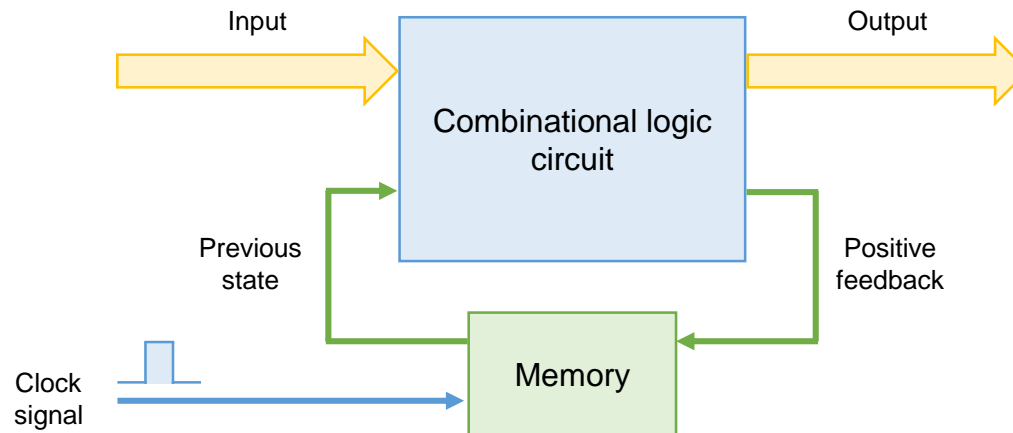
- **Sequential logic:** Logic circuit with memory built in
- Output is time-dependent: function of current inputs, previous inputs and previous outputs




SR Flip-flop

- **SR Flip-flop:** One-bit memory element with 2 inputs
- **Set input (S):** Active-low input, sets output (Q) to 1
- **Reset input (R):** Active-low input, sets output (Q) to 0

SR Flip-flop circuit


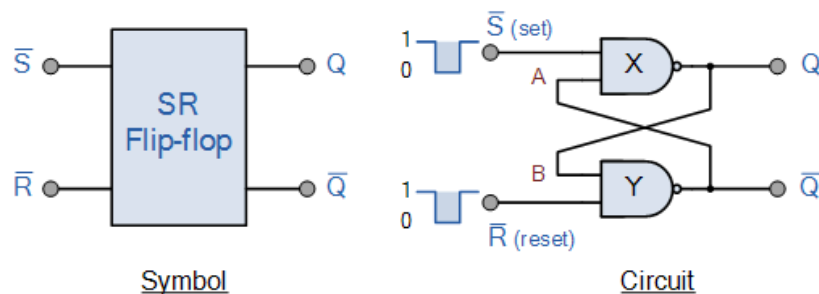


SR Flip-flop timing diagram

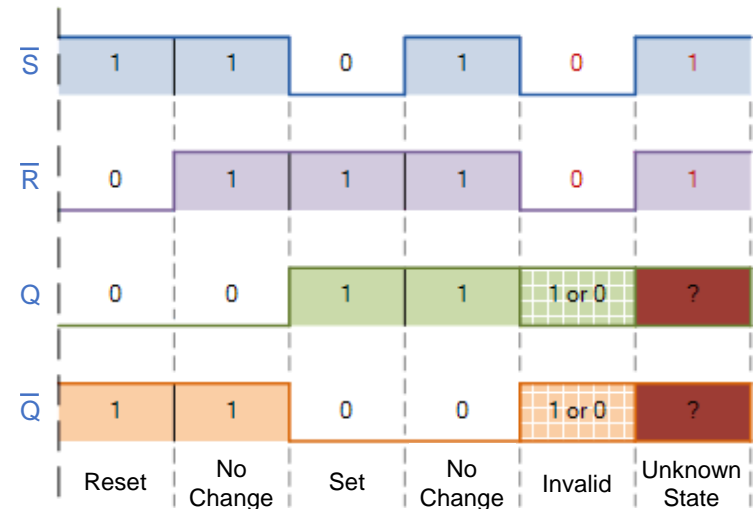

D Flip-flop

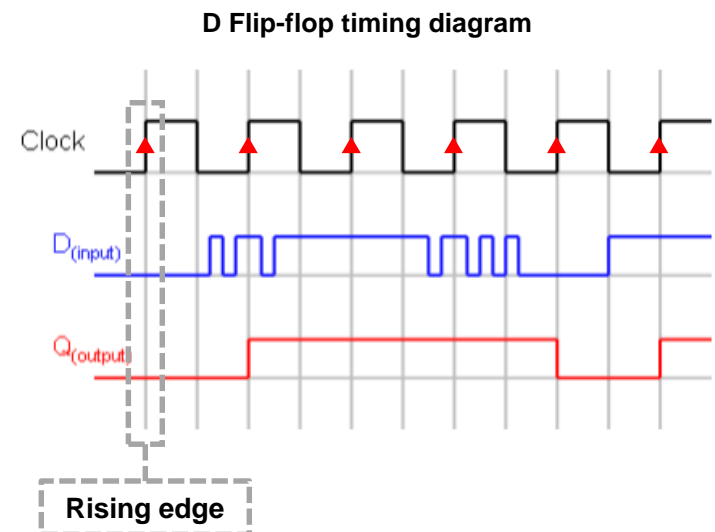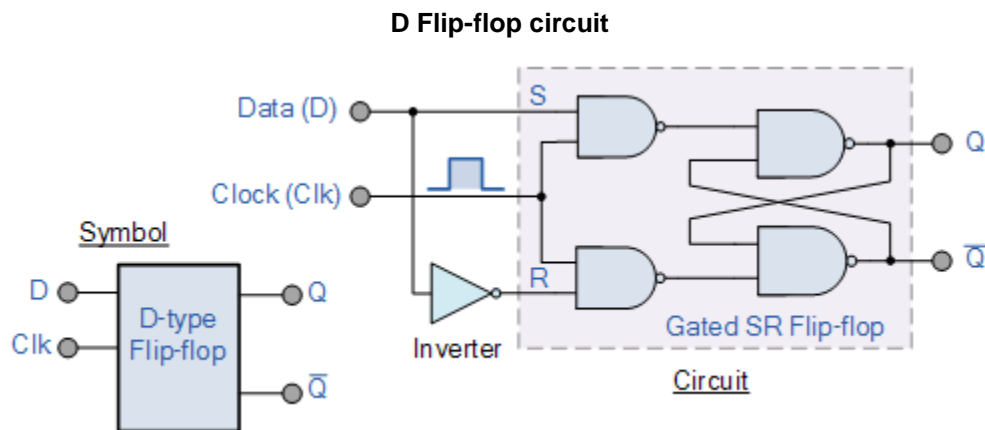
- **D Flip-flop:** One-bit memory element with 1 input
- Output takes the value of input at the **rising edge** of CLK
- Output stays constant until next rising edge



Shift register

- **Serial data:** Bits of data presented sequentially
- **Parallel data:** Bits of data presented concurrently
- **Shift register:** Converts data from serial to parallel

Shift register circuit

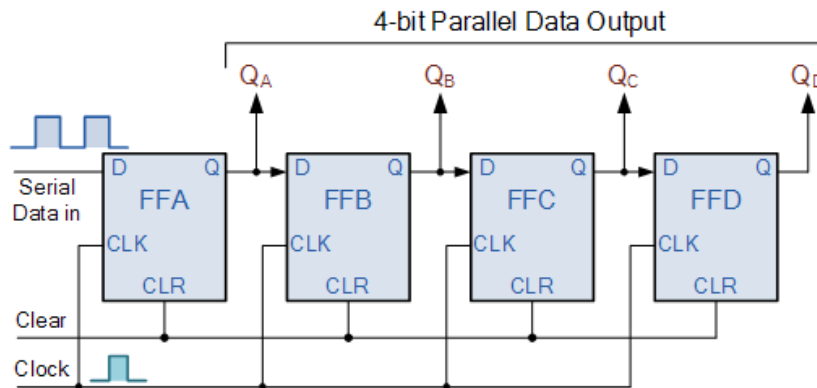


Shift register timing diagram



Power supplies and regulation


Power supplies

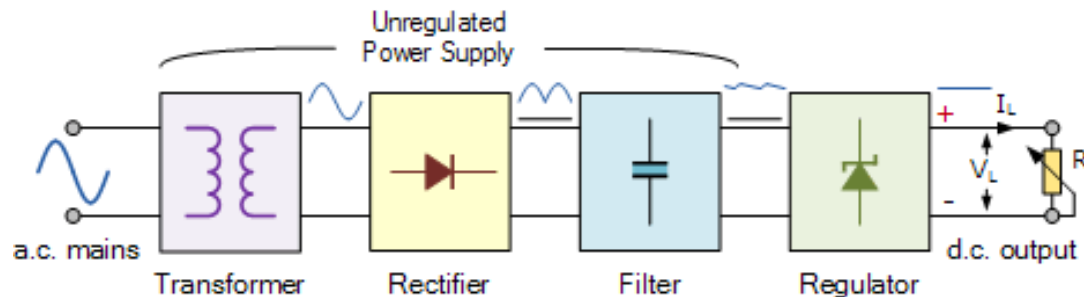- **Goal:** Convert AC line voltage (120V RMS) into a lower DC voltage usable with common components
- **Process:** Convert to lower voltage with transformer, rectify low voltage, apply regulation (optional) and filter
- May be either unregulated (easy) or regulated (less easy)
- May be either linear (inefficient) or switching (efficient)




Transformers

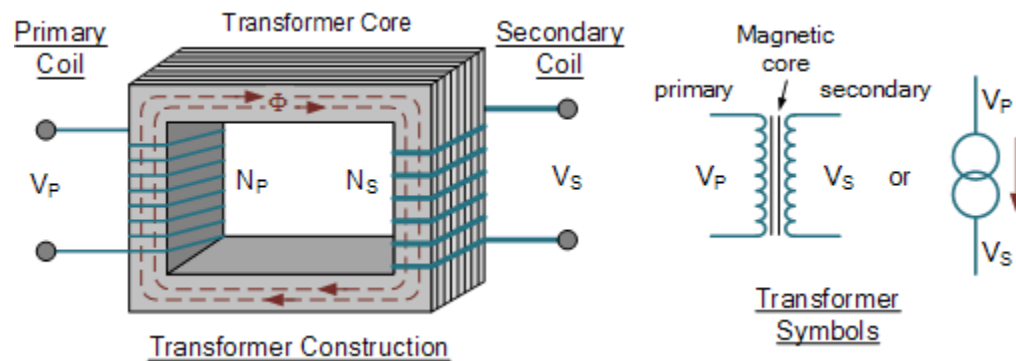
- **Transformer:** Converts from one AC voltage to another
- Conversion proportional to **turn ratio** ($N_S : N_P$)
- Output current calculated by **power conservation**



Transformers

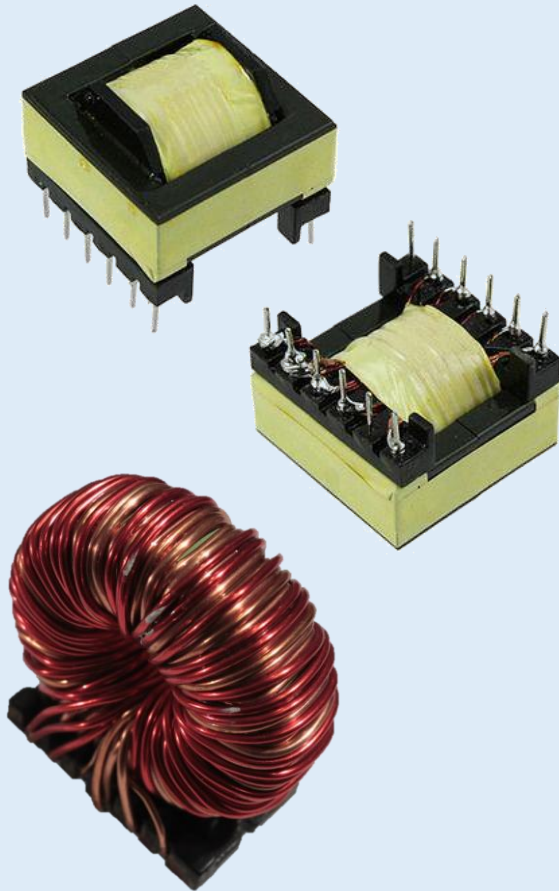



PCB-mounted

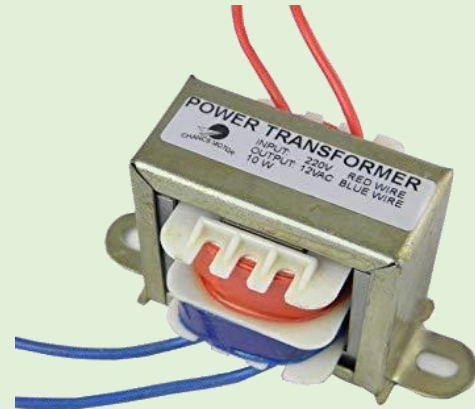


Chassis-mounted

Rectification

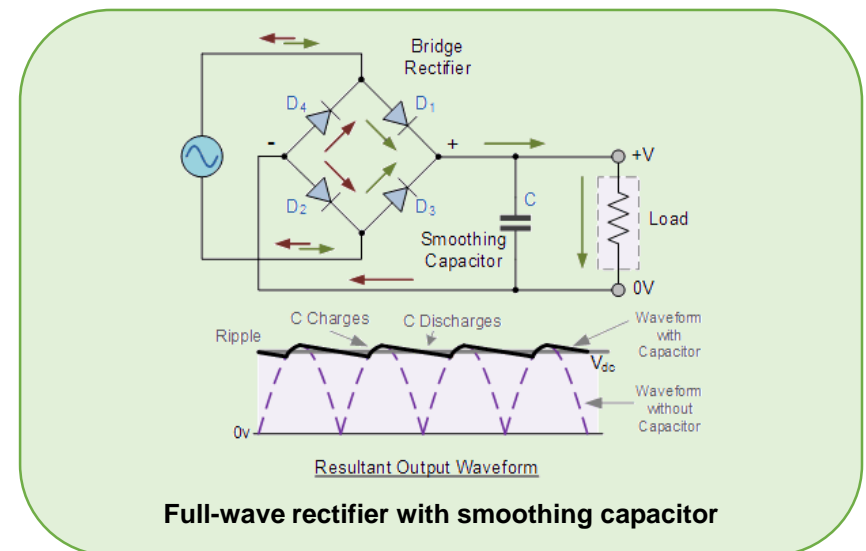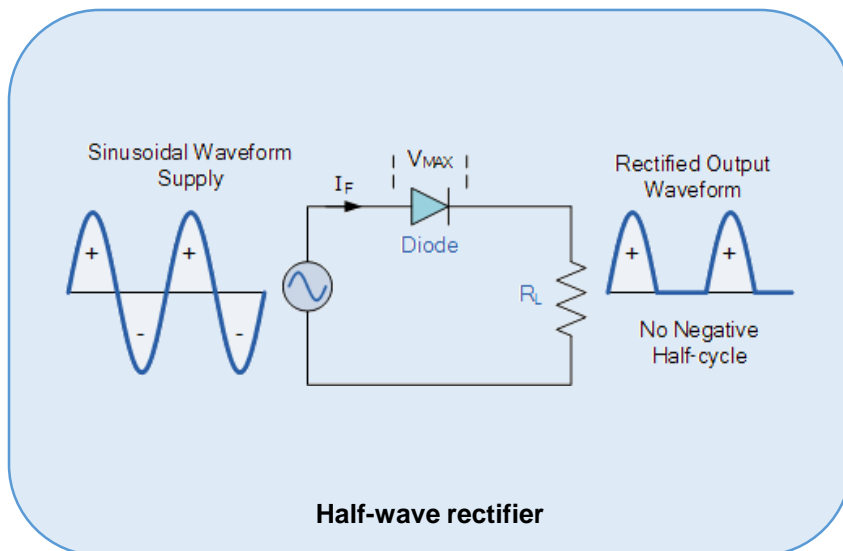
- **Rectifiers** convert AC voltages to DC
- Can be either half-wave (one diode) or full-wave (four diodes)
- Full-wave rectifiers use both half cycles of the AC input



Linear power supply

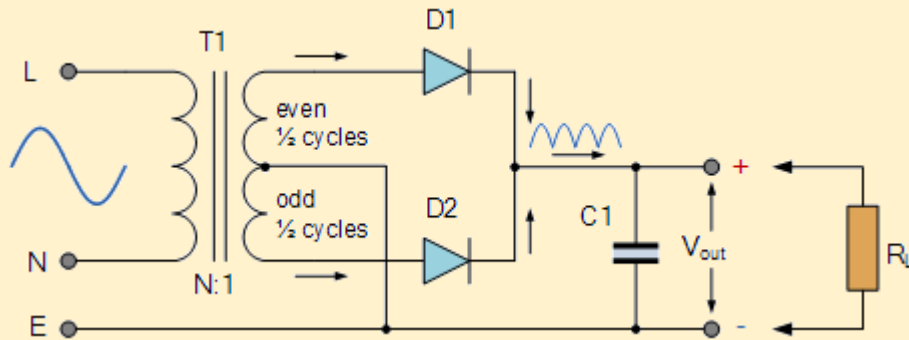

Unregulated power supply

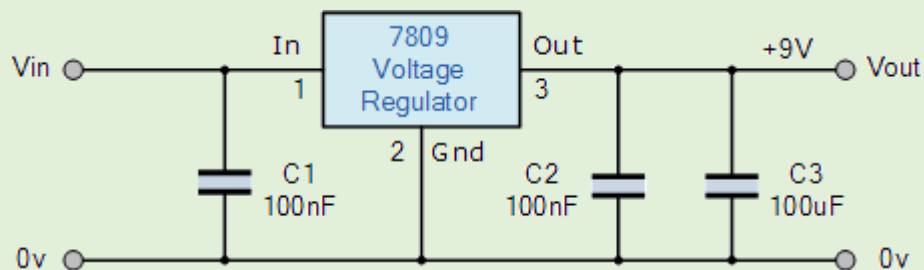

Voltage regulator

Unregulated power supply

- T1 converts AC line voltage into lower voltage AC
- **Center tap** of T1 placed in middle of secondary winding
- D1, D2 form a full-wave rectifier
- C1 filters output to produce DC




Voltage regulator

- LM78xx series: voltage regulator IC, available from 5V to 24V
- C1, C2, C3 are input and output filter capacitors
- Produces reliable DC voltage from unreliable transformer output


Switching power supply

- **Switching power supply:** Uses transistors (usually MOSFETs) to switch a transformer/inductor
- Much more **efficient** than linear power supplies, but extremely complicated to design
- May either step down (“**buck**”) or up (“**boost**”)

Switching “buck” converter

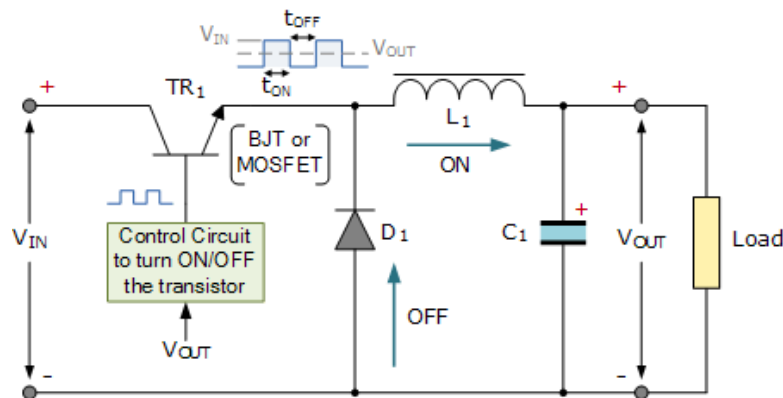


Switching “boost” converter

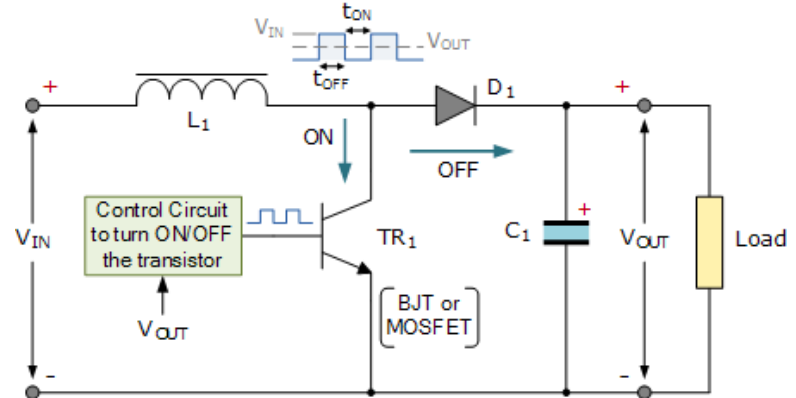

Supply filtering

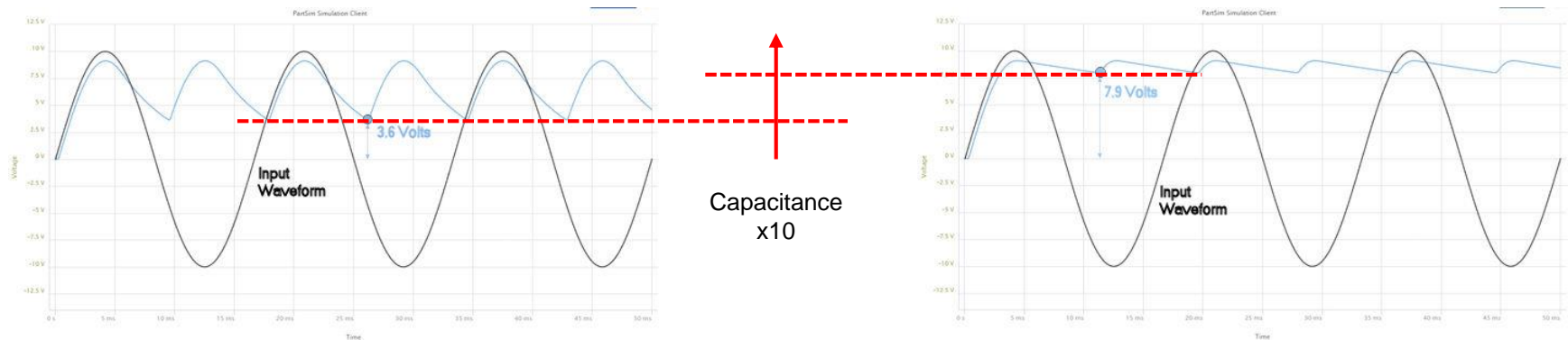- After rectification, supply must be **filtered** to get DC
- When combined with load and source resistance, output capacitor forms an RC low-pass filter (LPF)
- In general, larger capacitance = low cutoff frequency = **smoother output**




Design project overview

Project description

- **Goal:** Understand how simple blocks can be combined to make a complex system
- **Function:** Infrared (IR) remote-controlled audio amplifier
- **Main components:** power supply, digital lock, audio amplifier, IR receiver, IR transmitter (separate PCB)
- IR receiver/transmitter are optional, only if time allows



Block diagram

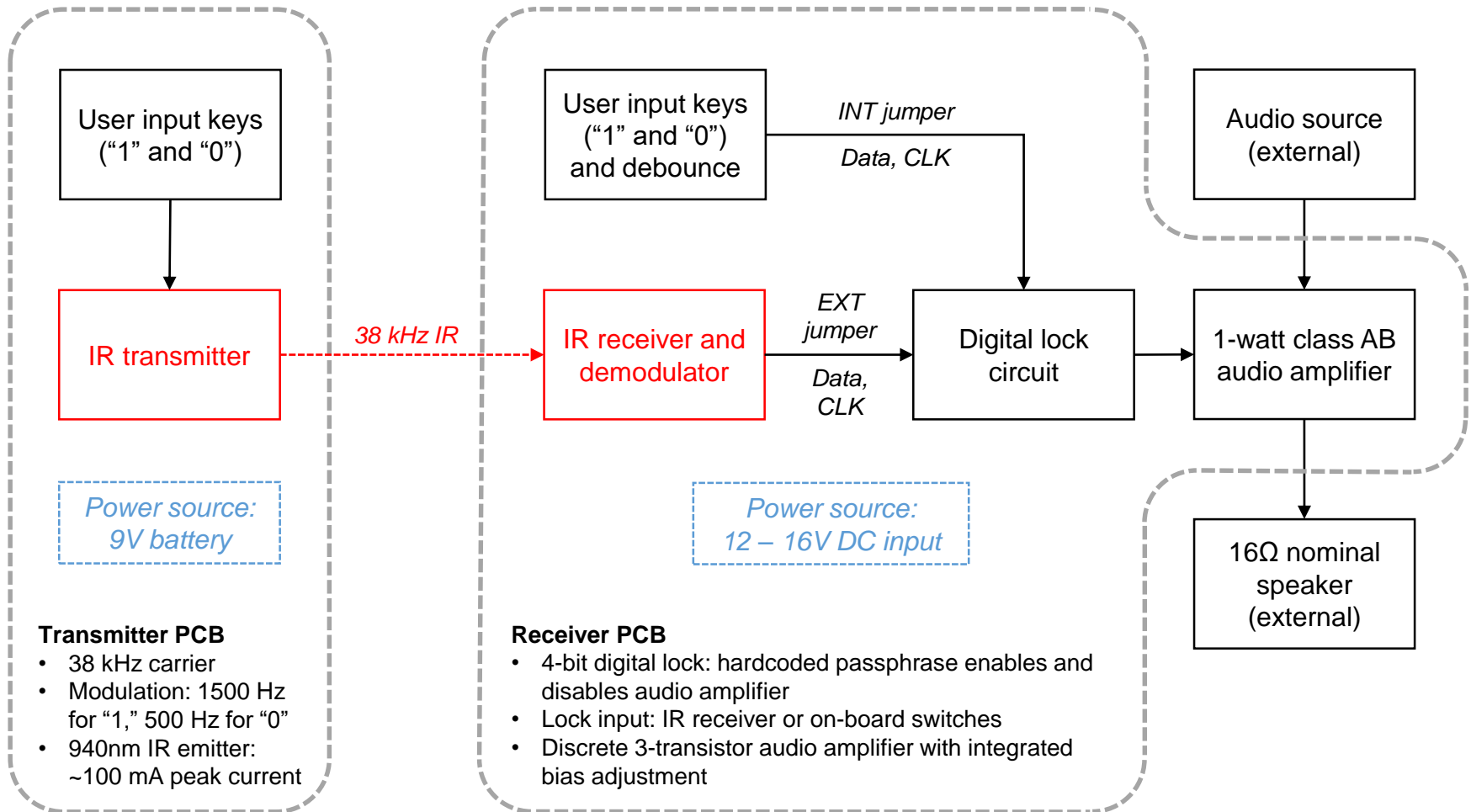


Project schedule

- **Lab 3 (1/22 – 1/23):** Power supply and digital lock
- **Lab 4 (1/27 – 1/28):** Audio amplifier
- **Lab 5 (1/29 – 1/30):** IR receiver/transmitter (optional), finish any remaining sections
- Project not graded for completeness, only required to attend all lab sessions


Receiver PCB

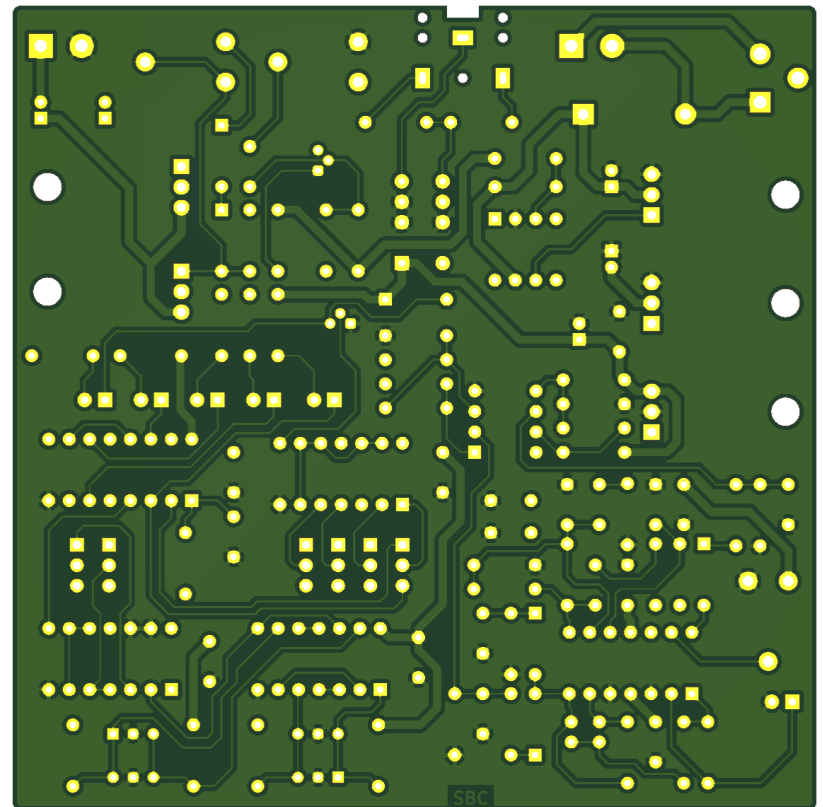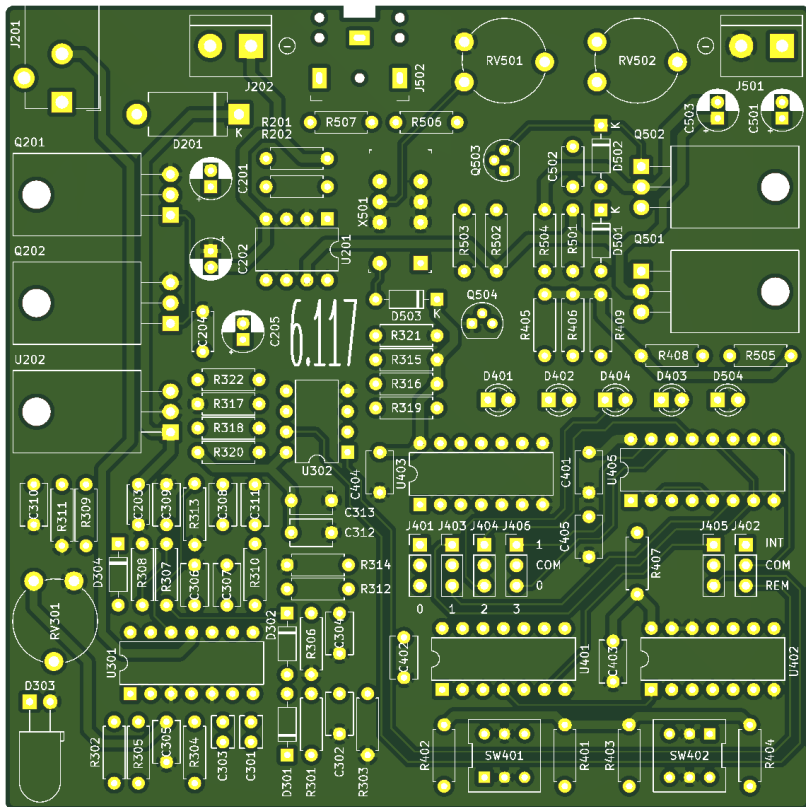


Receiver PCB

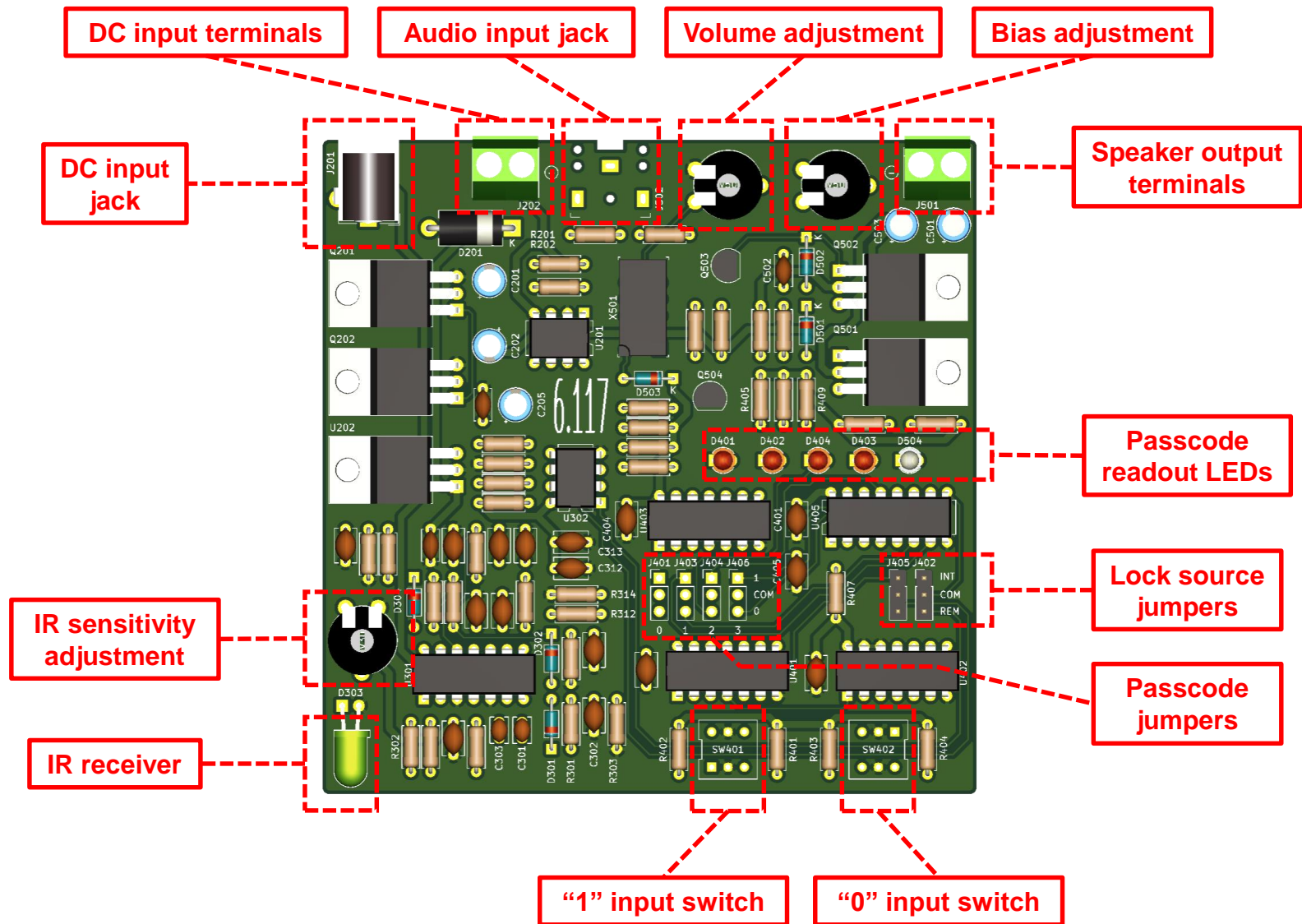

Transmitter PCB

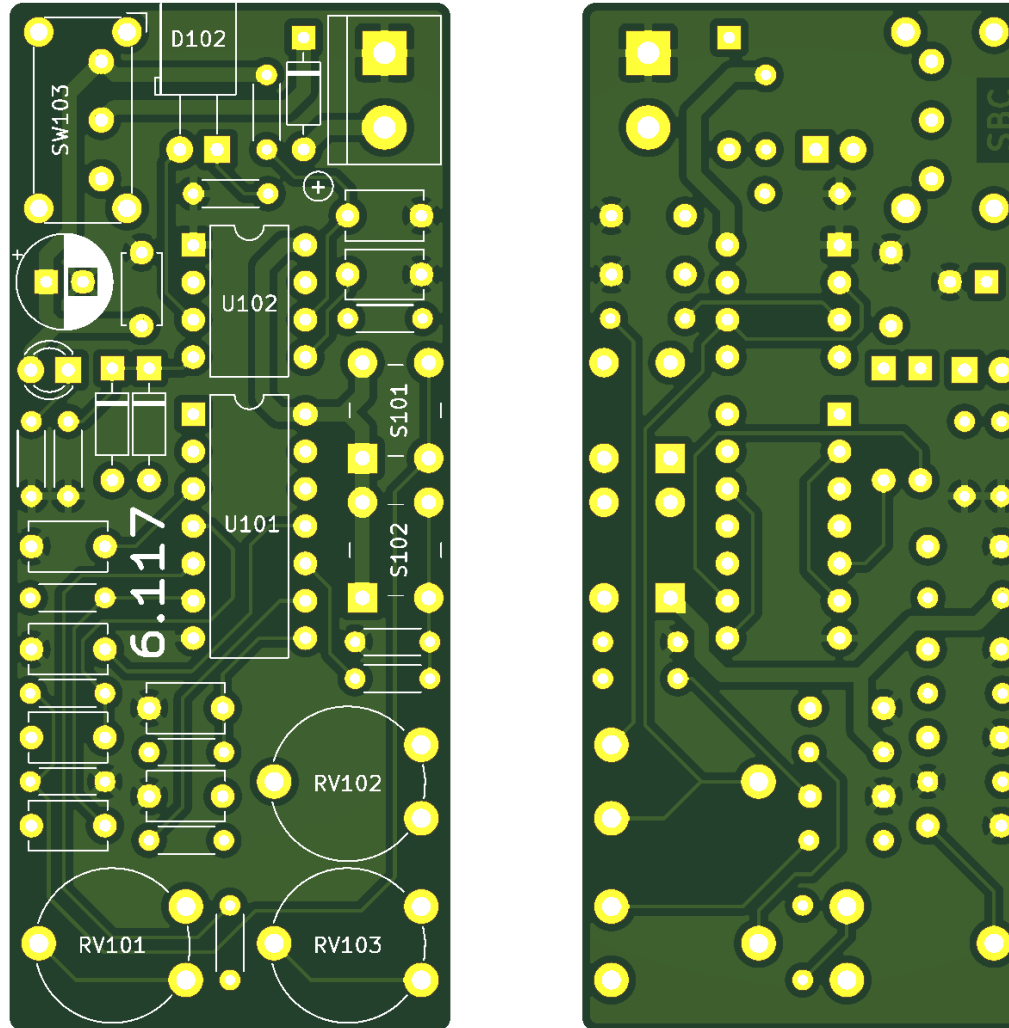


Transmitter PCB

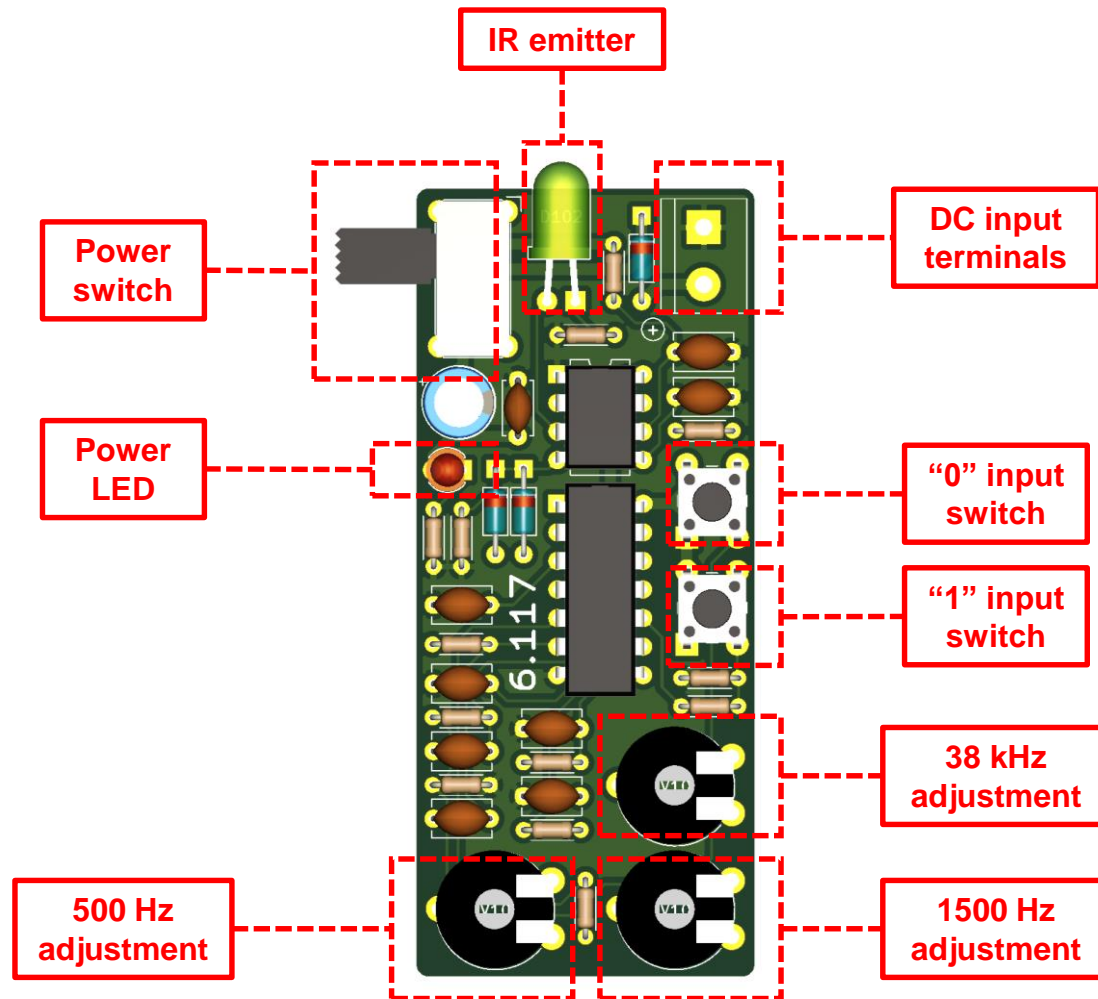

Lab 3 overview


LM7805 Voltage regulator

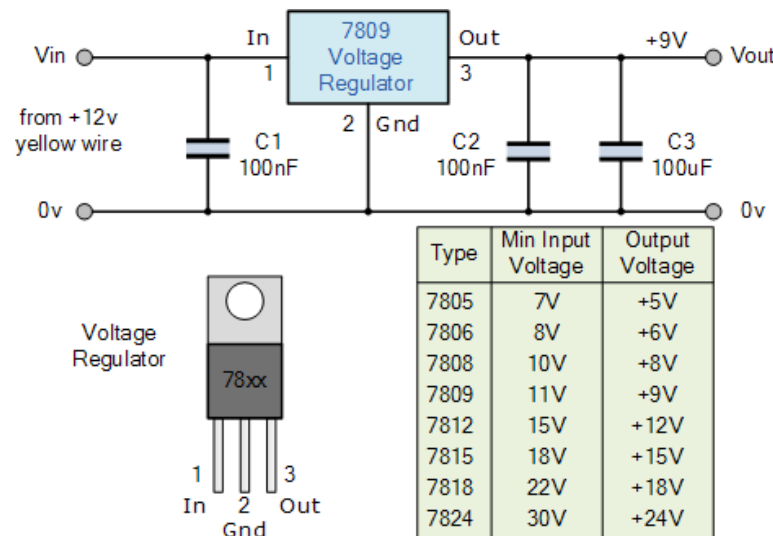- **LM7805:** Integrated linear voltage regulator
- Conveniently provides supply regulation in one package
- Use **input/output capacitors** to avoid oscillation



Power supply circuit

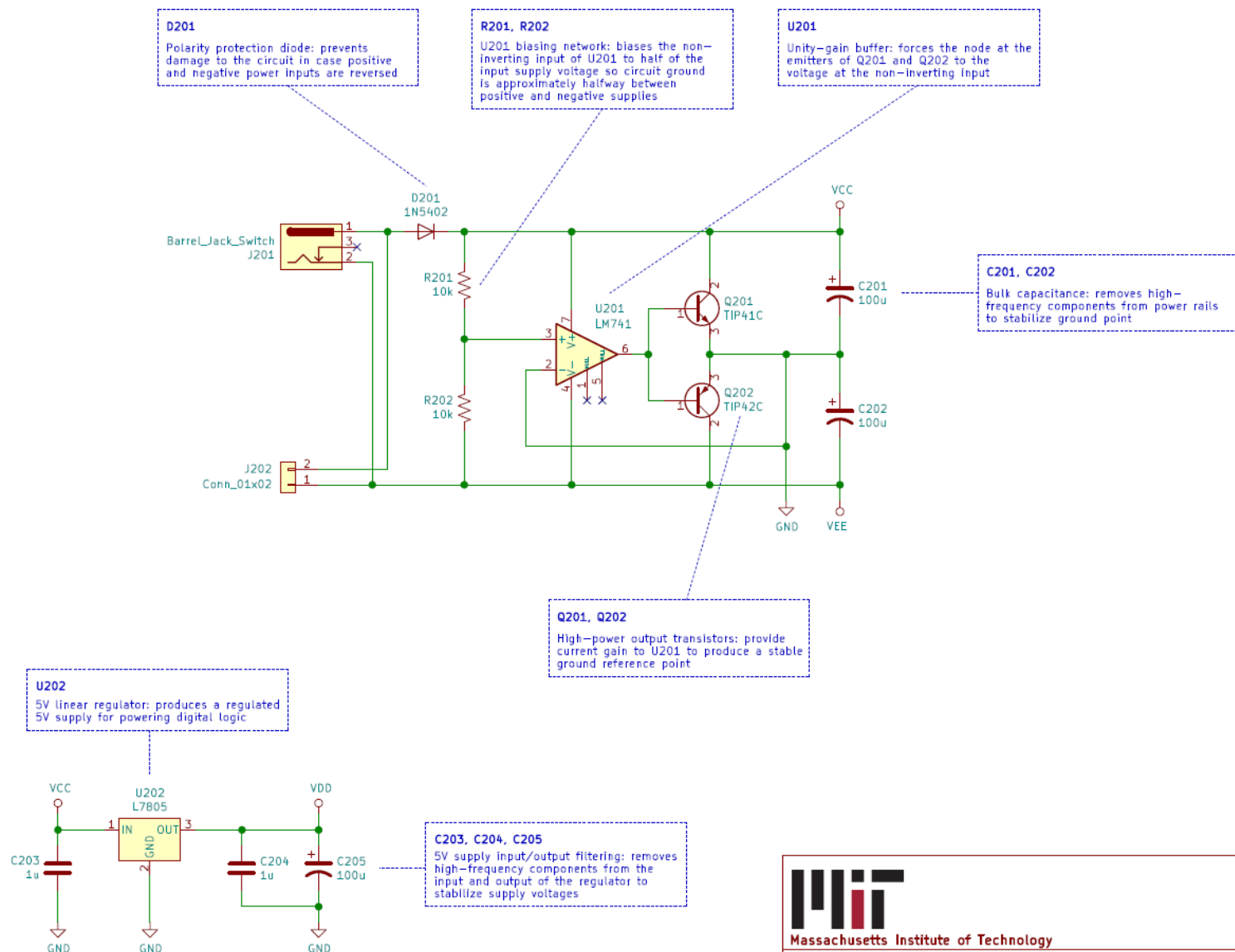- **Function:** Generates $\pm 6V$ and $+5V$ power supplies
- Uses non-inverting op-amp with push-pull output to generate **floating ground**
- Uses LM7805 to generate **regulated** $+5V$ supply
- Contains **protection diode** to prevent damage



Massachusetts Institute of Technology

Sheet: /Power/

File: power.sch

Title: 6.117 Final Project: Receiver


Size: USLetter Date: 1/15/2020

KiCad E.D.A. kicad (5.1.5)–3

Rev: A.0.1


Id: 5/5

Power supply components

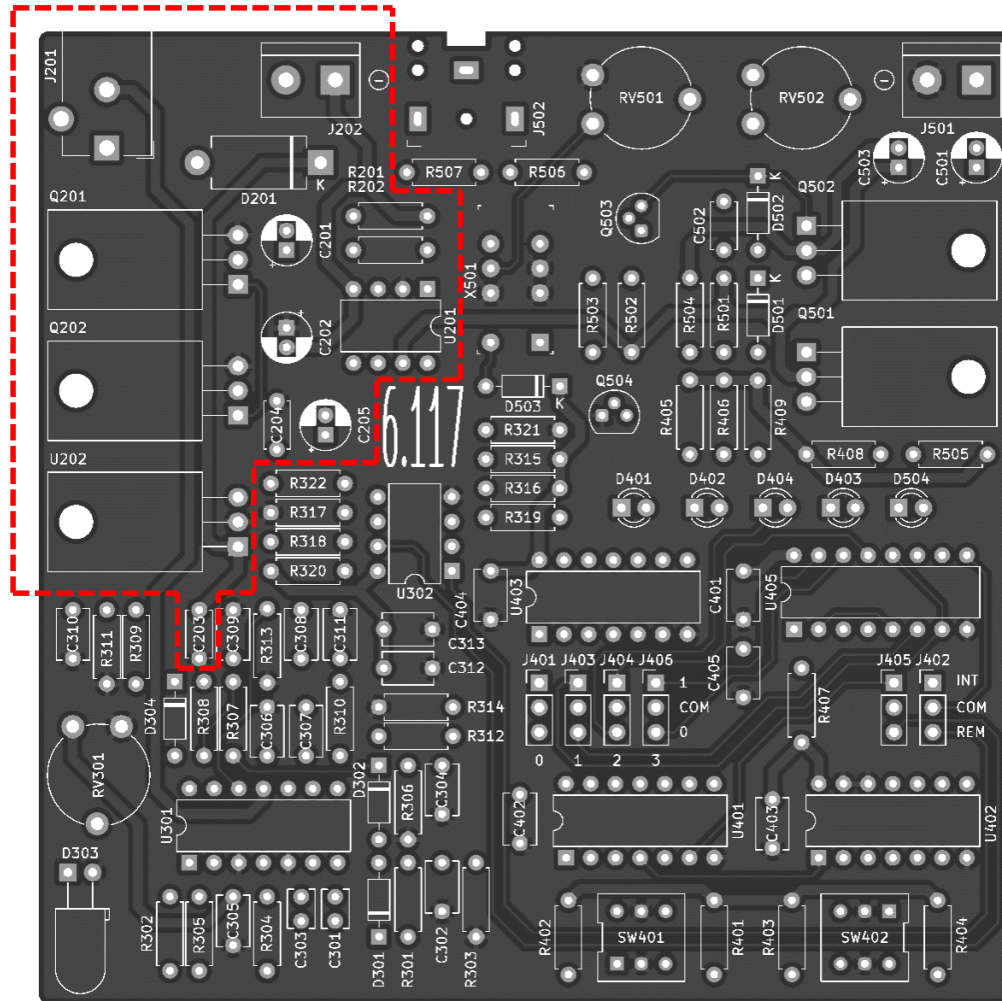

Digital lock circuit

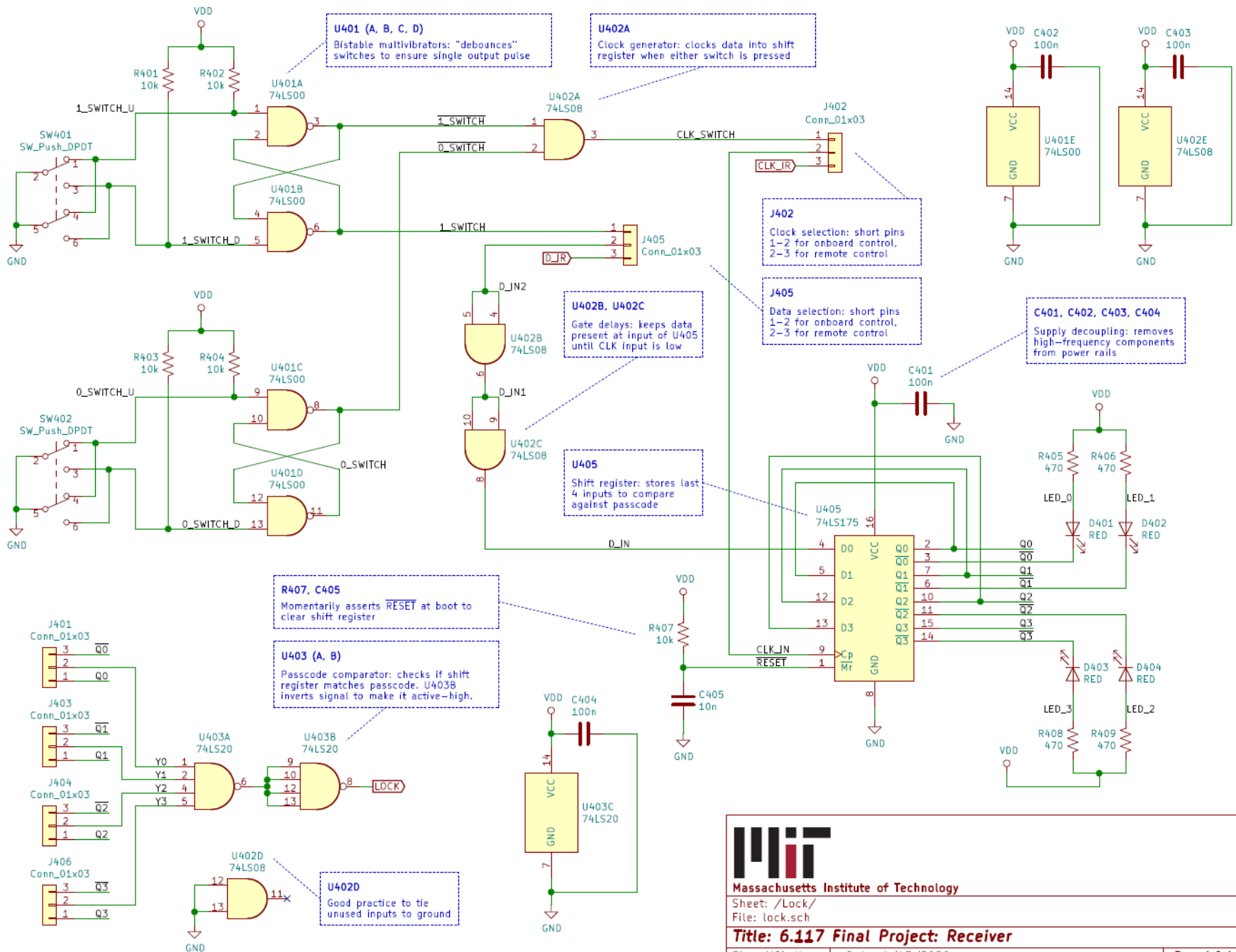- **Function:** “Unlock” amplifier when passcode is sent
- Uses **shift register** to keep track of received data
- Four-bit passcode hardcoded in via **jumper wires**
- Selectable input source: **buttons or IR receiver** (optional)



Massachusetts Institute of Technology

Sheet: /Lock/

File: lock.sch

Title: 6.117 Final Project: Receiver


Size: USLetter Date: 1/15/2020

KiCad E.D.A. kicad (5.1.5)-3

Rev: A.0.1

Id: 3/5

Digital lock components


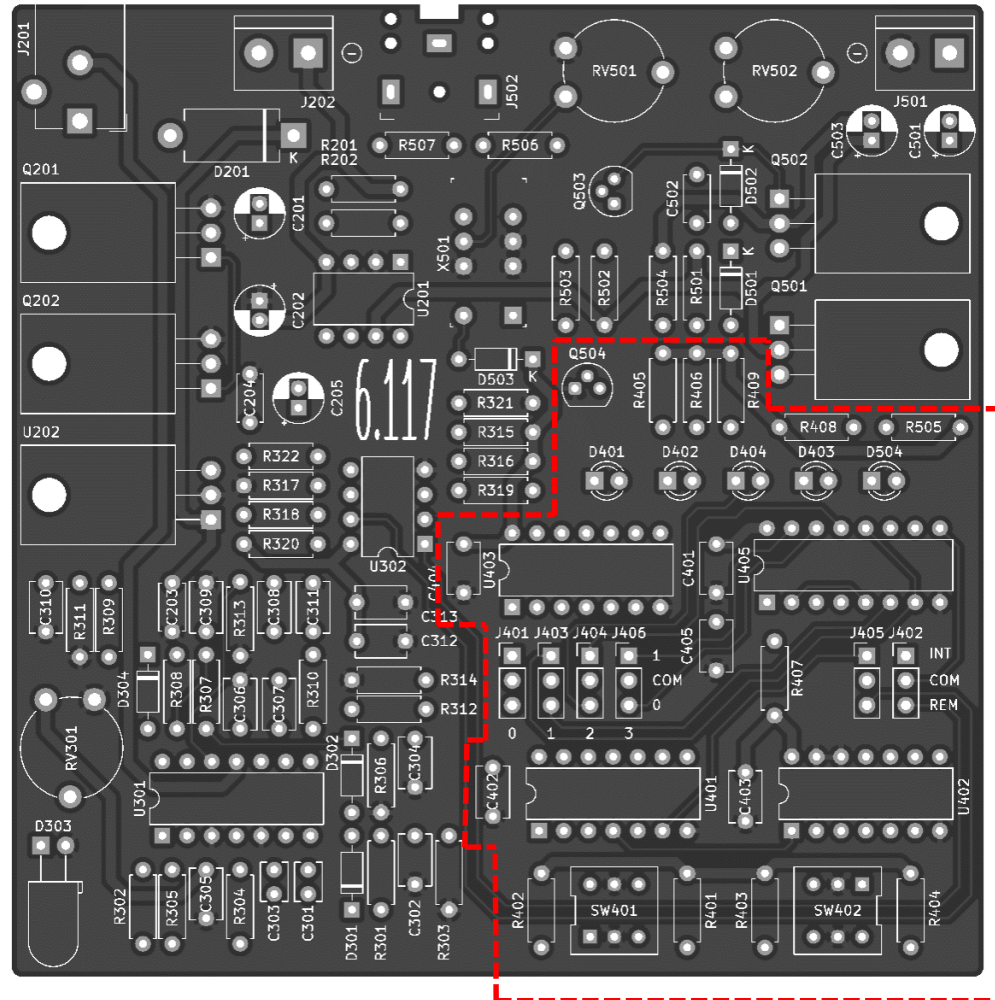


Assembly


- Fold leads **under PCB** so they don't fall out
- Solder from **short to tall** components
- Attach power transistors with **screws/nuts** and thermal pad before soldering
- Ask someone to check your PCB **before soldering**

Soldering technique

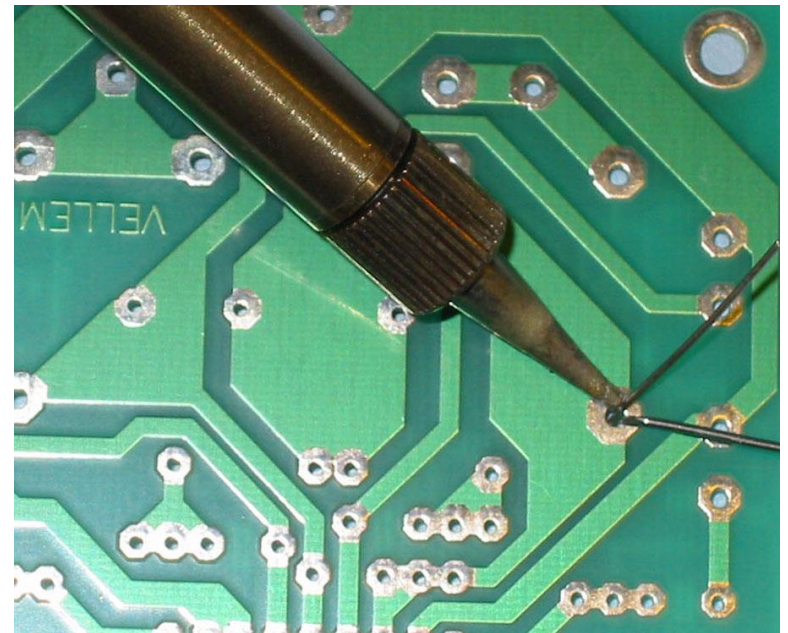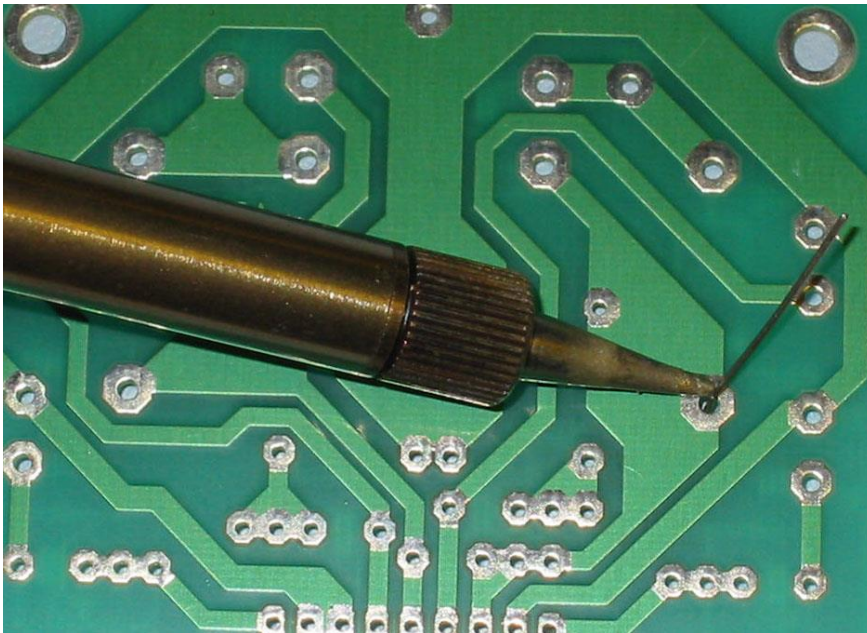- Apply the soldering iron to the **component** first, then feed the solder into the joint
- Some components take longer to heat than others



Soldering technique

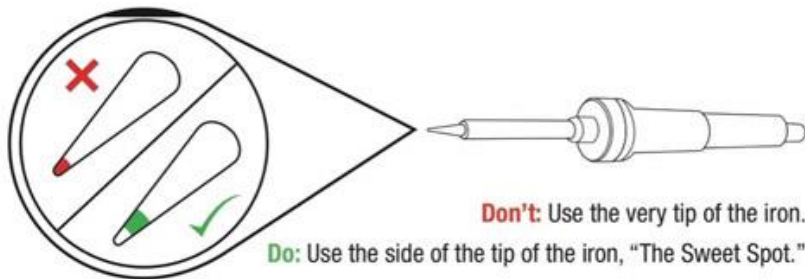

Do: Touch the iron to the component leg and metal ring at the same time.



Do: While continuing to hold the iron in contact with the leg and metal ring, feed solder into the joint.



Don't: Glob the solder straight onto the iron and try to apply the solder with the iron.



Do: Use a sponge to clean your iron whenever black oxidation builds up on the tip.



A

Solder flows around the leg and fills the hole - forming a volcano-shaped mound of solder.



B

Error: Solder balls up on the leg, not connecting the leg to the metal ring.
Solution: Add flux, then touch up with iron.



C

Error: Bad Connection (i.e. it doesn't look like a volcano)
Solution: Flux then add solder.




D

Error: Bad Connection...and ugly...oh so ugly.
Solution: Flux then add solder.



E

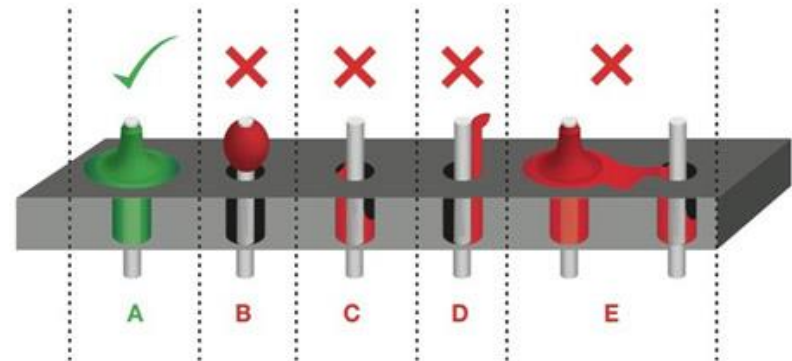Error: Too much solder connecting adjacent legs (aka a solder jumper).
Solution: Wick off excess solder.



Soldering video

